


**Kirchoff's Laws, Wheatstone Bridge,
Meter Bridge**

03.06.09

By R. S. Saini

(M.Sc. Physics, M.Ed.)

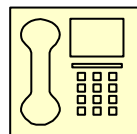Kendriya Vidyalaya, Sector 47, Chandigarh




9417071540

KIRCHHOFF'S LAWS:

I Law or Current Law or Junction Rule:

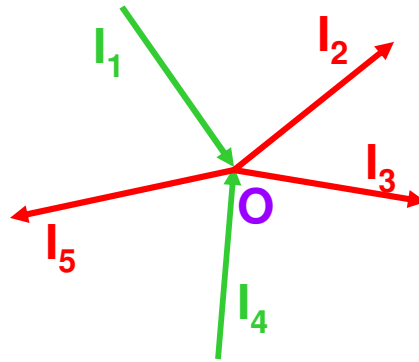The algebraic sum of electric currents at a junction in any electrical network is always zero.



$$I_1 - I_2 - I_3 + I_4 - I_5 = 0$$


Sign Conventions:

1. The **incoming currents** towards the junction are taken **positive**.
2. The **outgoing currents** away from the junction are taken **negative**.

Note: The charges cannot accumulate at a junction. The number of charges that arrive at a junction in a given time must leave in the same time in accordance with conservation of charges.

II Law or Voltage Law or Loop Rule:

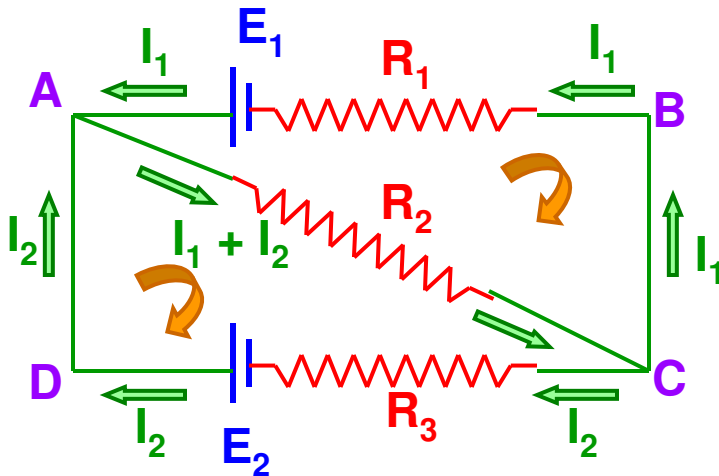The algebraic sum of all the potential drops and emf's along any closed path in an electrical network is always zero.



Loop ABCA:

$$- E_1 + I_1 \cdot R_1 + (I_1 + I_2) \cdot R_2 = 0$$

Loop ACDA:

$$- (I_1 + I_2) \cdot R_2 - I_2 \cdot R_3 + E_2 = 0$$

Sign Conventions:

1. The emf is taken **negative** when we traverse from **positive** to **negative** terminal of the cell through the electrolyte.
2. The emf is taken **positive** when we traverse from **negative** to **positive** terminal of the cell through the electrolyte.

The potential **falls** along the **direction** of current in a current path and it **rises** along the **direction** opposite to the current path.

3. The potential **fall** is taken **negative**.
4. The potential **rise** is taken **positive**.

Note: The path can be traversed in **clockwise** or **anticlockwise** direction of the loop.

Wheatstone Bridge:

Currents through the arms are assumed by applying Kirchhoff's Junction Rule.

Applying Kirchhoff's Loop Rule for:


Loop ABDA:

$$-I_1 \cdot P - I_g \cdot G + (I - I_1) \cdot R = 0$$

Loop BCDB:

$$-(I_1 - I_g) \cdot Q + (I - I_1 + I_g) \cdot S + I_g \cdot G = 0$$

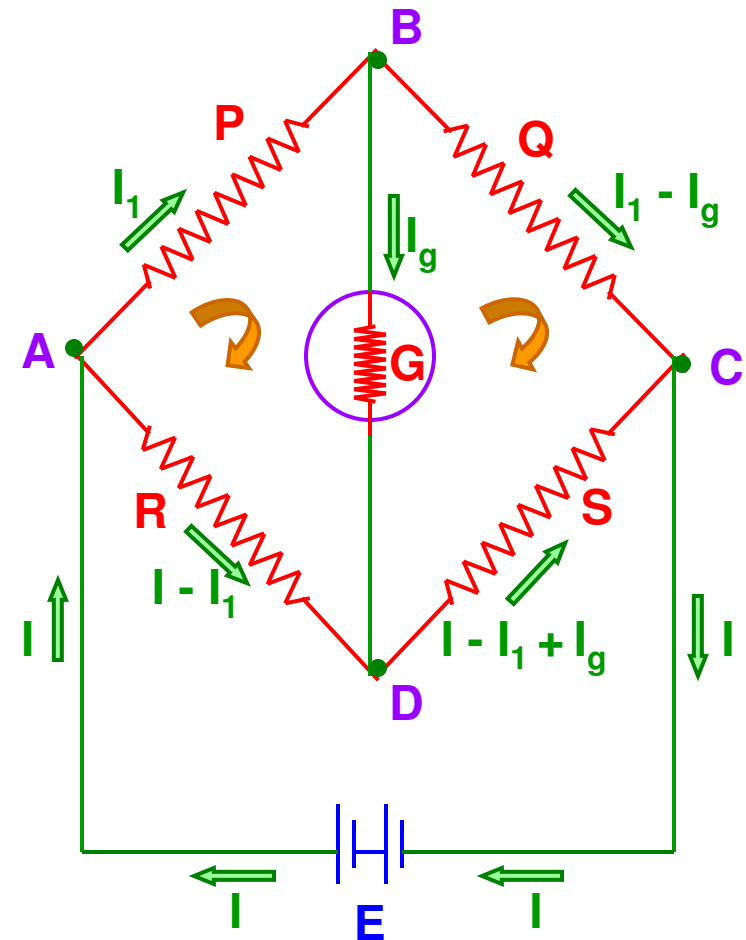When $I_g = 0$, the bridge is said to be balanced.




By manipulating the above equations, we get

$$\frac{P}{Q} = \frac{R}{S}$$

Metre Bridge:

Metre Bridge is based on the principle of Wheatstone Bridge.

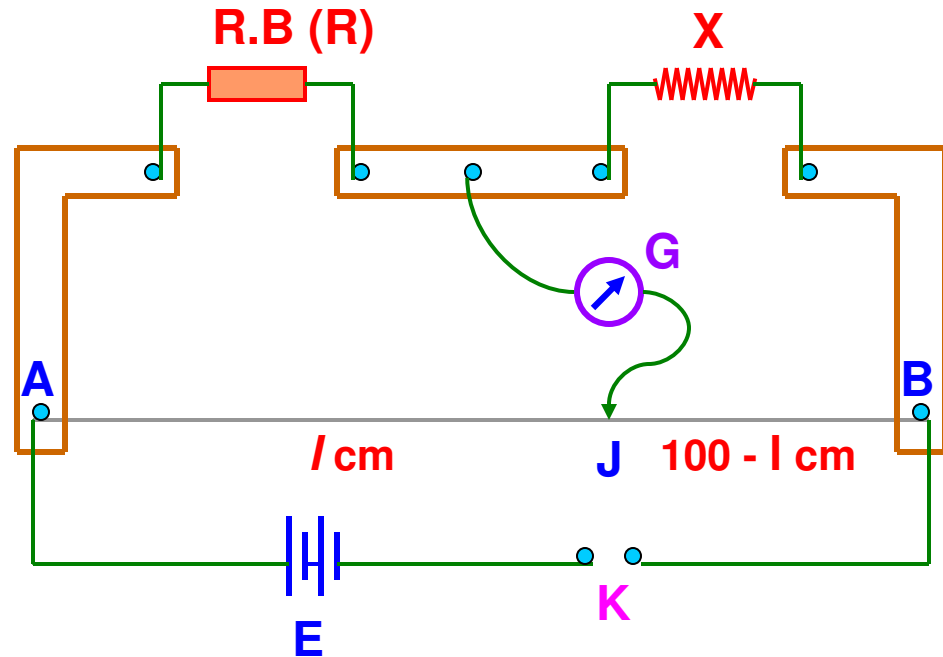When the galvanometer current is made zero by adjusting the jockey position on the metre-bridge wire for the given values of known and unknown resistances,



$$\frac{R}{X} = \frac{R_{AJ}}{R_{JB}} \quad \longrightarrow \quad \frac{R}{X} = \frac{AJ}{JB} \quad \longrightarrow \quad \frac{R}{X} = \frac{l}{100 - l}$$

(Since, Resistance \propto length)

Therefore, $X = R (100 - l) / l$