


Series LCR circuit

05.06.09

By R. S. Saini



(M.Sc. Physics, M.Ed.)

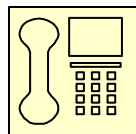Kendriya Vidyalaya, Sector 47, Chandigarh




9417071540

Series L-C-R Circuit

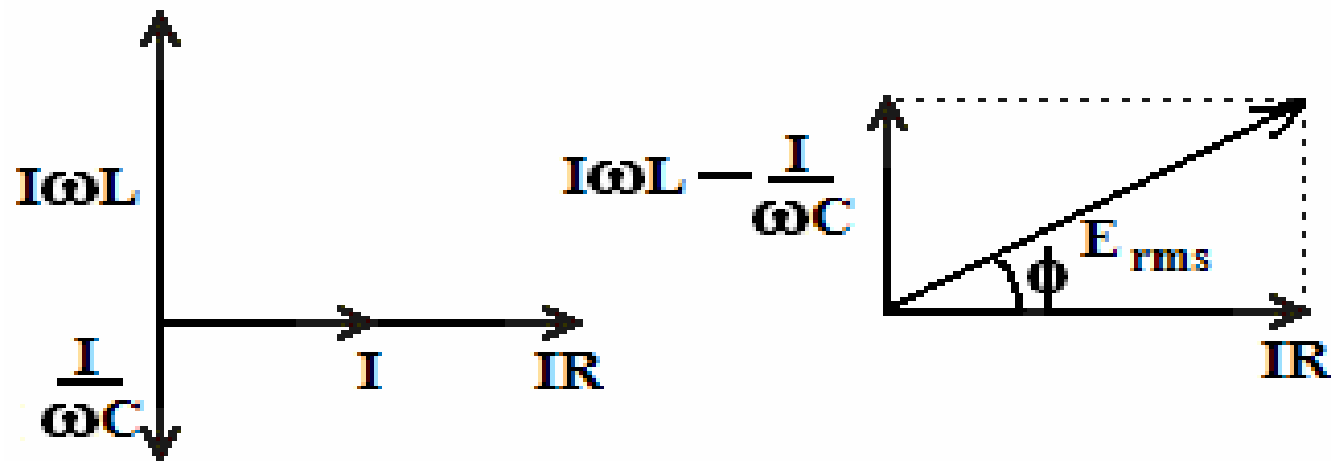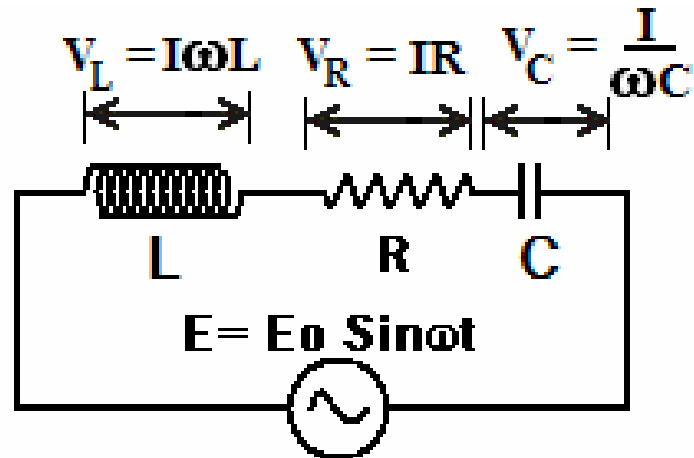

Impedance

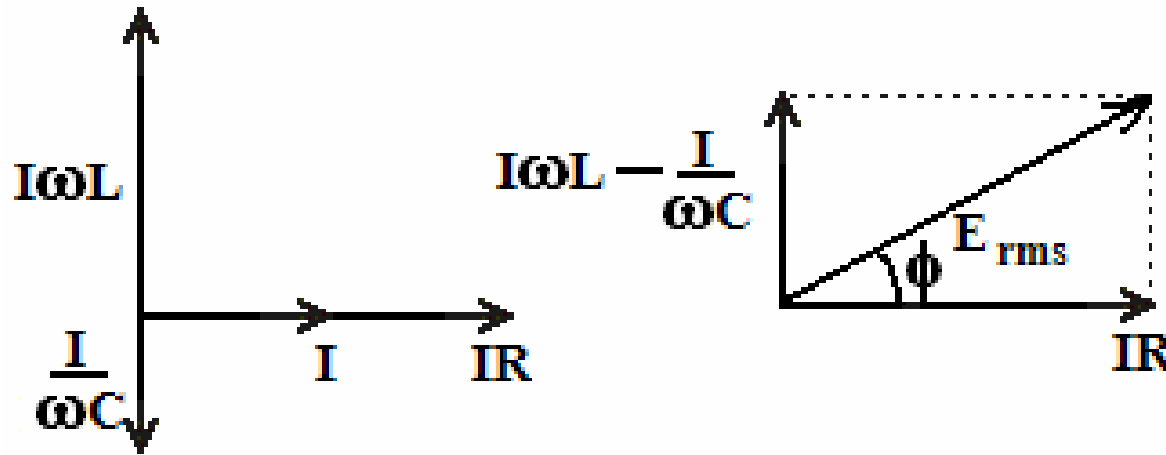


$$E = \sqrt{I^2 R^2 + \left(I\omega L - \frac{I}{\omega C} \right)^2} = \sqrt{I^2 R^2 + I^2 \left(\omega L - \frac{1}{\omega C} \right)^2}$$

$$= I \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C} \right)^2} = I \sqrt{R^2 + (X_L - X_C)^2}$$

$$\text{or } I = \frac{E}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C} \right)^2}} \text{ OR } \frac{E}{\sqrt{R^2 + (X_L - X_C)^2}}$$


$\sqrt{R^2 + (X_L - X_C)^2}$ is called impedance and denoted by 'z', has unit ohm

Phase difference between current

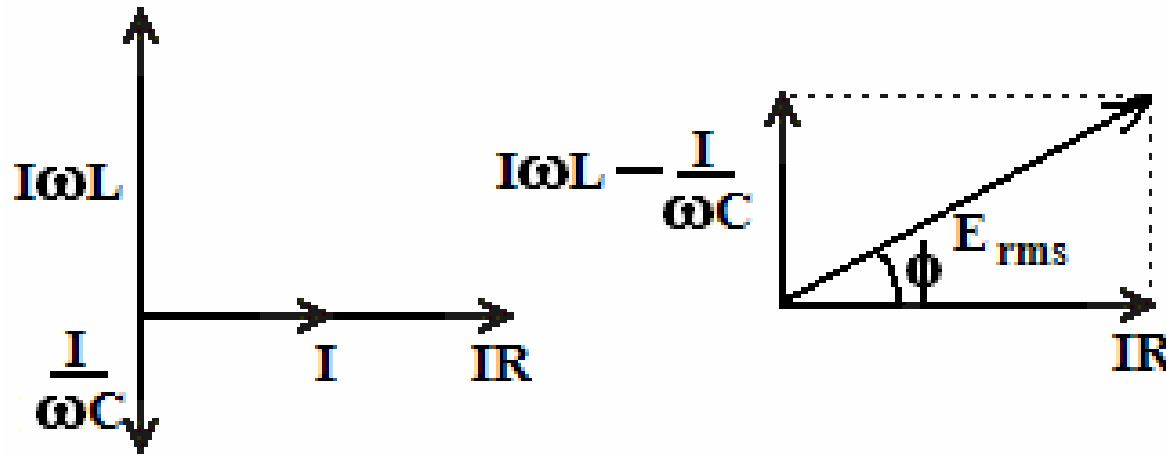


$$\tan \phi = \frac{I \left(\omega L - \frac{1}{\omega C} \right)}{IR} \quad \text{or} \quad \phi = \tan^{-1} \left[\frac{\omega L - \frac{1}{\omega C}}{R} \right] = \tan^{-1} \frac{X_L - X_C}{R}$$

Variation of impedance with frequency

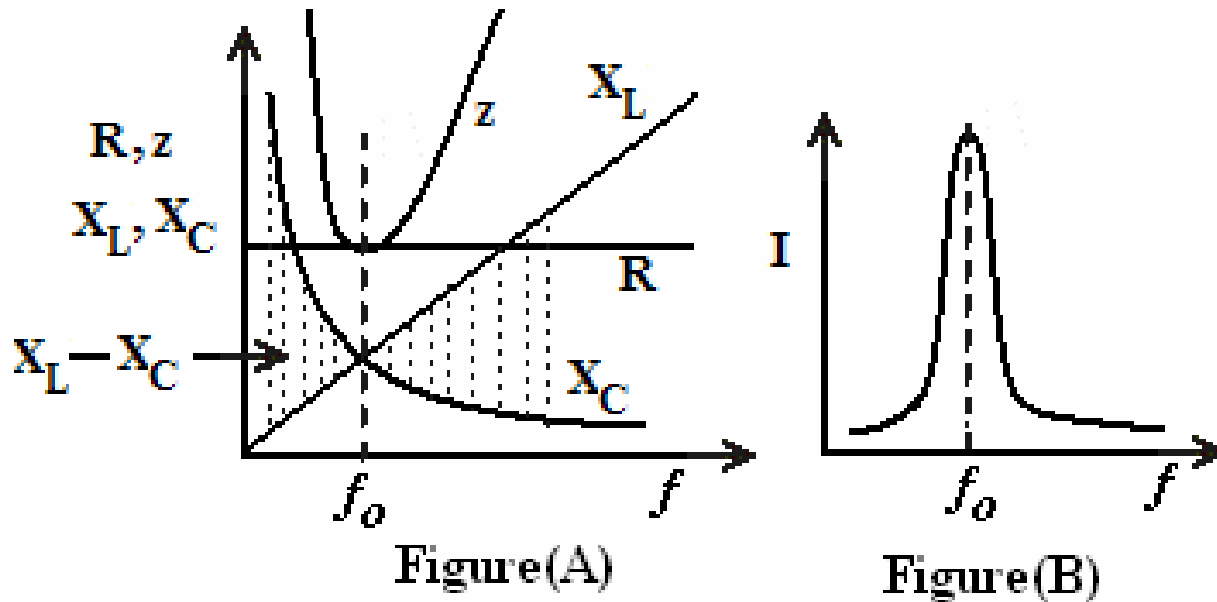

Resonance

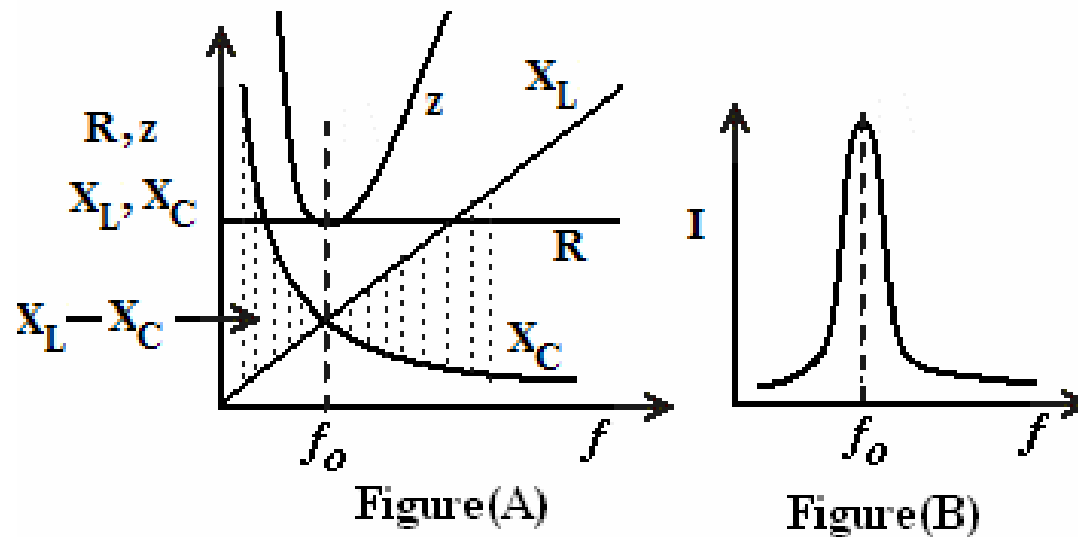

$$z = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2} \text{ would be minimum when } \omega L = \frac{1}{\omega C}$$

$$\text{or } \omega^2 = \frac{1}{LC} \text{ or } \omega = \frac{1}{\sqrt{LC}} \text{ or } 2\pi\nu = \frac{1}{\sqrt{LC}} \text{ or } \boxed{\nu = \frac{1}{2\pi\sqrt{LC}}}$$

and minimum value of 'z' is = R and current is maximum = $\frac{E}{R}$